



Guru Aanklan

**GRAND
TEST**

**ELECTRONICS PAPER - II
HSC DIGITAL ELECTRONICS
PAPER - [A]**

**Duration : 3 Hrs
M.M. : 50**

Q.1A Select the correct alternatives and rewrite. (4M)

- (1) For mod 150 counter, flip-flops required are -----
(A) 10 (B) 15 (C) 8 (D) 9
- (2) In ----- if $A = 0$, $B = C$, then output $Y = C$
(A) ORgate (B) NAND gate (C) NORgate (D) EX-ORgate
- (3) ----- is sequential access secondary storage.
(A) Floppy disk (B) Hard disk (C) magnetic tape (D) none of the above
- (4) In T-Flipflop the output frequency is -----
(A) same as input frequency (B) one half of its input frequency
(C) double of its input frequency (D) none of above

B Attempt any two of the following. (6M)

- (1) Subtract the following binary numbers using 1's complement method:
(A) $(11010)_2 - (11011)_2$ (B) $(11011)_2 - (1101)_2$
- (2) How J-K flip-flop is constructed by using R-S flip-flop? Write its truth table.
- (3) Write a note on EBCDIC code.

Q.2A Attempt two of the following (6M)

- (1) What is a register? Give any 4 applications of registers
- (2) Draw the diagram of 4-bit left shift register using D flip-flop and explain the working
- (3) Solve the following:
(A) $(25)_{10} = (\dots)_2$ (B) $(C5)_{16} = (\dots)_{10}$ (C) $(69)_{10} = (\dots)_{BCD}$ (D) $(B7C)_{16} = (\dots)_2$

B Attempt any one the following (4M)

- (1) Draw block diagram of computer and explain function of each block.
- (2) Write a note on Shift register

Q. 3A Attempt any two of the following (6M)

- (1) Define Counter. State the applications of counters. State types of counters.
- (2) Implement the logic expression using a multiplexer IC which has inverted inputs such as IC 74150. $f(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 12, 14)$
- (3) Explain the working of Ring Counter using D flip-flops.

B Attempt any one the following (4M)

- (1) Draw logic diagram and symbol of clocked R-S flip-flop. Explain its working with the help of truth table. Write its limitation (disadvantage).
- (2) Explain the working of edge triggered T flip-flop.

Q.4A Attempt any two of the following (6M)

- (1) State various types of volatile memories.
- (2) Draw the logic circuit for the Boolean expression
$$Y = (A + B) \cdot (\overline{A \cdot B})$$
. Write the truth table and name the gates used

- (3) Explain the working of CMOS NOR gate with necessary circuit diagram

B Attempt any one the following (4M)

- (1) Draw and explain basic circuit of CMOS NAND gate.
- (2) State types of D/A converters. Explain the working of any one type and state its disadvantages.

Q.5A Attempt any two of the following (6M)

- (1) Explain successive approximation type ADC.
- (2) Explain the working of counter type A/D converter.
- (3) Define half-adder in Boolean algebra. Explain the table of combinations for half-adder.

B Attempt any one of the following (4M)

- (1) Draw logic diagram of decade counter and explain its working.
- (2) What are the types of secondary memory devices?

OR

Q.5A Attempt any Two of the following (6M)

- (1) What is logic family? Give different types of logic families.
- (2) Draw and explain TTL inverter (NOT) circuit.
- (3) Explain the concept of 1-bit memory cell.

B Attempt any one of the following (4M)

- (1) Draw the logic diagram for following Boolean expression using basic gates only. Write its truth table.
- (2) What will be the output voltage of 4-bit R-2R ladder for binary input $(1011)_2$. Given logic 0 = 0V and logic 1 = 3.2 volts.